

**Third Semester B. Tech. (Electronics and Communication Engineering)
Examination**


ANALOG CIRCUITS DESIGN

Time : 3 Hours]

[Max. Marks : 50

Instructions to Candidates :—

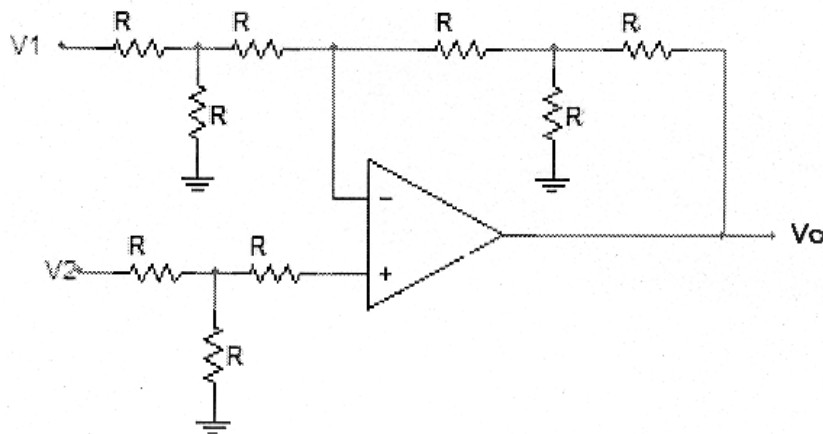- (1) All questions are compulsory.
 - (2) All questions carry marks as indicated against them.
 - (3) Assume suitable data and illustrate answers with neat sketches wherever necessary.
-
1. (a) Derive the DC equations for Dual input balanced output differential amplifier.
5(CO1)
 - (b) Elaborate the importance of Level shifter circuit in Differential amplifier.
5(CO1)
-
2. (a) For the circuit shown in Fig. 2, find V_o in terms of V_1 and V_2 .



5(CO2)

- (b) Design a practical differentiator circuit to differentiate a sine wave signal of $1 \sin (628.31)t$. Sketch the input-output waveform. 5(CO2,4)
3. (a) Design a R-C phase shift oscillator using op-amp to oscillate at 500 Hz. 5(CO2,3,4)
- (b) Design a second order active high pass Butterworth filter with lower cut-off frequency 10 KHz. 5(CO5)
4. (a) For Schmitt trigger circuit using op-amp, evaluate threshold voltages V_{UT} , V_{LT} hysteresis voltage, and centre of hysteresis curve. Assume op-amp with saturation voltage ± 12 V, $R_1 = 2 \text{ K}\Omega$, $R_2 = 4 \text{ K}\Omega$, $V_{ref} = -4$ V. 5(CO2,3)
- (b) Explain the operation of Sample and hold circuits. 5(CO2)
5. (a) Design an astable multivibrator using IC555 having output frequency 5 KHz and 60% duty cycle. 5(CO5)
- (b) Illustrate block diagram of Phase lock loop and explain its working in brief. 5(CO2)

