

**Fourth Semester B. Tech. (Electronics and Communication Engineering) Examination**

**ANALOG CIRCUITS**

Time : 3 Hours ]

[ Max. Marks : 60

**Instructions to Candidates :—**

- (1) All questions carry marks as indicated.
- (2) Assume suitable data wherever necessary.

1. Consider the circuit shown in Fig. 01.

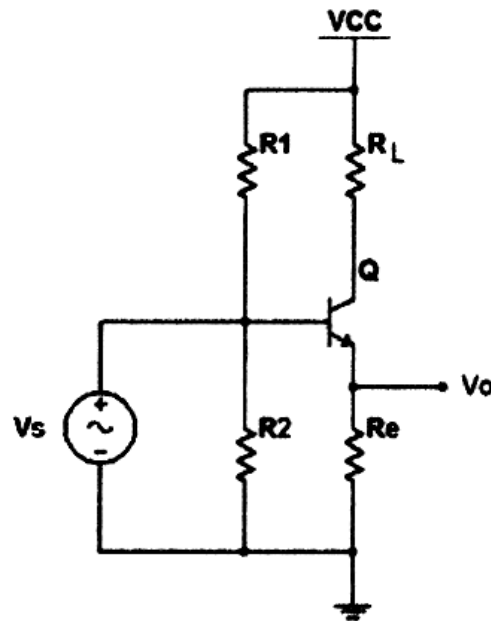


Fig. 1

- (a) Identify the feedback topology used in the amplifier. Justify. 2(CO1)
- (b) Analyze the amplifier to calculate equations for voltage gain, input resistance and output resistance of the amplifier circuit. 8(CO2)

2. (a) Elaborate mathematically the effect of load coupling in class A power amplifier. 8(CO3)  
 (b) Explain cross-over distortion. 2(CO1)
3. (a) Explain working of Hartley oscillator. 6(CO2,3)  
 (b) Determine the oscillation frequency and feedback fraction for a transistorized Hartley oscillator having  $L_1 = L_2 = 100 \mu\text{H}$  and  $C = 20 \text{ pF}$ . 4(CO2,3)
4. (a) Derive gain, input resistance and output resistance of a dual input balanced output differential amplifier. 8(CO3)  
 (b) Explain the use of swamping resistor in differential amplifier. 2(CO3)
5. (a) Design a Schmitt trigger using OP-AMP to obtain threshold voltage  $V_{ut}$  and  $V_{lt}$  as  $+1 \text{ V}$  and  $-1.4 \text{ V}$  respectively. Assume supply voltage of  $\pm 12 \text{ V}$  and input of  $1 \text{ kHz}$ ,  $4 \text{ Vpp}$ . Sketch input and output waveforms. 6(CO4)  
 (b) Design a circuit using OP-AMP to implement following input output relation :  

$$V_o = -V_a - 2V_b - 2.5V_c$$
 4(CO4)
6. (a) Design a square wave generator using IC 555 having an output frequency of  $1 \text{ kHz}$ . 5(CO5)  
 (b) Design a second order LPF using OP-AMP with high cut-off frequency of  $2 \text{ kHz}$ . 5(CO5)

