

Course Code : ECT 251

KQLR/RS – 24 / 1543

**Third Semester B. Tech. (Electronics and Communication Engineering)
Examination**

ELECTRONIC DEVICES


Time : 3 Hours]

[Max. Marks : 60

Instructions to Candidates :—

- (1) Assume suitable data wherever necessary.
- (2) All questions are compulsory.

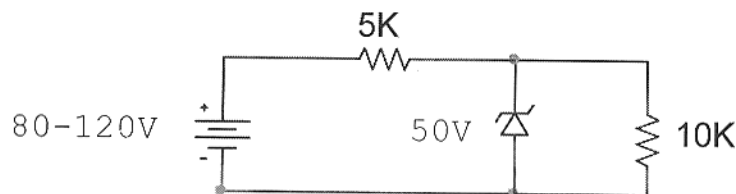1. (a) For the circuit shown below, Evaluate the maximum and minimum values of Zener diode current. Also find P_{Zmax} .




5(CO1,5)

- (b) A full wave rectifier circuit design with two identical silicon diodes with a forward resistance of $10\ \Omega$ each. A d.c. voltmeter connected across the load of $1\ K\Omega$ reads $60\ V$. Calculate :
 - (i) Percentage efficiency.
 - (ii) Ripple factor of FWR.
 - (iii) Transformer voltage rating.
- 5(CO1,5)
2. (a) Draw the input, output and transfer characteristics of transistor operated in Common Emitter configuration. Derive an expression of output collector current.
- 4(CO1)

KQLR/RS-24 / 1543

Contd.

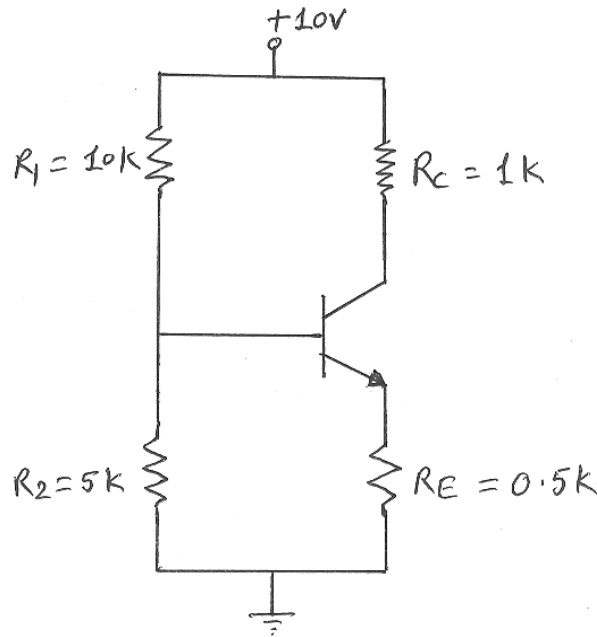- (b) Determine the collector current and collector voltage of silicon transistor operated in CE mode with Self bias circuit shown below, Assume $\beta = 100$.



Page 1 of 2

6(CO4,5)

3. (a) A Common Emitter amplifier with voltage divider bias has $R_1 = 100 \text{ K}\Omega$, $R_2 = 10 \text{ K}\Omega$, $R_C = 5 \text{ K}\Omega$ and $R_S = 10 \text{ K}\Omega$. Draw hybrid model for the voltage divider bias. Use following h-parameters and estimate A_v , A_p , input and output impedances.

$$h_{ie} = 1100 \text{ }\Omega, h_{re} = 2.5 \times 10^{-4}, h_{fe} = 50, h_{oe} = 25 \text{ }\mu\text{A/V.}$$

8(CO4,5)

- (b) Draw h-parameter equivalent model for the common base configuration.

2(CO1)

4. (a) The FET amplifier with $I_{DSS} = 15 \text{ mA}$, $V_p = -6 \text{ V}$. Determine the drain current for $V_{GS} = -3 \text{ V}$.

5(CO4,5)

- (b) Describe the use of FET as a voltage variable resistance.

5(CO2)

5. (a) Discuss depletion and enhancement type MOSFETs in respect of working and C-V characteristics. Also write their individual applications. 6(CO2)
- (b) What do you mean by body effect in MOSFET devices ? 4(CO2)
6. (a) Implement the equation using CMOS logic :
- $$X = (A + B) (C + D) + E \quad 6(\text{CO3})$$
- (b) Draw and discuss voltage transfer characteristics of CMOS inverter. Define V_{IH} and V_{IL} . 4(CO2,3)

